

# PW2 Addendum: State Space Averaging for Advanced Digital Control of Power Converters

**Kip Haggerty, Ph.D., P.E.**

***H&A* Systems  
Engineering**  
**Controls • Communications • Sensors**

P.O. Box 2875 • El Segundo, CA 90245  
(310) 607-9609 • <http://www.hasys.com/>

**Download at: <http://www.hasys.com/tutorials.html>**

# Outline

---


- **Design Approach**
- **State Space Averaging Methodology**
- **Buck Converter Example**
- **Advanced Algorithms**

# Recall Our Design Approach

---

- **Analyze “Plant” (i.e. the Power Converter) in Analog (Continuous Time) Domain**
  - Look for Type of Controller Needed
- **Select Feedback Controller (PID, PI, Integrator, LPF, etc.)**
- **Analyze Continuous Time Closed Loop System with Pure Time Delay**
  - Is Processing Interval Short Enough to Provide Desired Bandwidth?
- **Convert Feedback Controller to Discrete Time**
  - Check Digital Resolution
  - Check for Numerical Problems in Computations
  - Check if Resolution Expansion by Averaging is Required
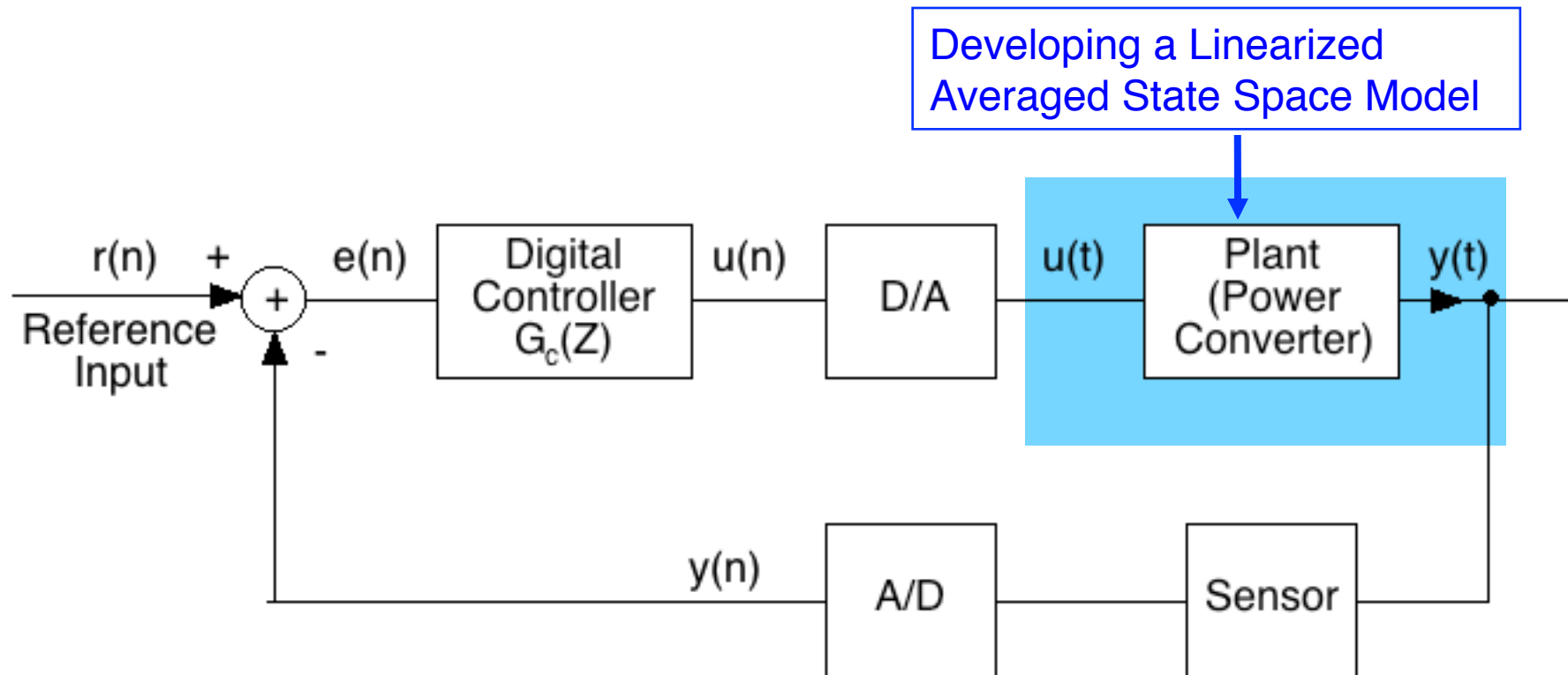
# Modeling Plant Required to Predict Performance



- **References:**

- Daniel M. Mitchell, DC-DC Switching Regulator Analysis, NY, McGraw-Hill, 1988. See Chapter 4.
- [SB] Rudolf P. Severns and Gordon (Ed) Bloom, Modern DC-to-DC Switchmode Power Converter Circuits, NY, Van Nostrand, 1985. See Chapters 2 and 3.

# Plant Analysis Requires State Space Averaging and Small Signal Linearization

---

- **Develop First Order Matrix Differential Equations for Each Set of Switch Settings**
  - Eq 1 On/Off for CCM and DCM
  - Eq 2 Off/On for CCM and DCM
  - Eq 3 Off/Off for DCM Only
- **Take Average of Equations**  $\longrightarrow \sum_i d_i \cdot [Eq]_i$ 
  - $d_i$  is the duty time in the  $i$ th case
  - Justified by High Switching Frequency
- **Linearize Averaged Equation Via Small Signal Approximation**
  - i.e. Linearize about DC Operating Point
  - Assume Any Product of Two ac Terms is Negligible
  - NOTE: Approximation May Be Invalid - Simulation/Prototyping
- **References:**
  - Daniel M. Mitchell, DC-DC Switching Regulator Analysis, NY, McGraw-Hill, 1988. See Chapter 4.
  - [SB] Rudolf P. Severns and Gordon (Ed) Bloom, Modern DC-to-DC Switchmode Power Converter Circuits, NY, Van Nostrand, 1985. See Chapters 2 and 3.

# Reminder: Circuit --> Linear Differential Equations --> Laplace Transform Algebraic Equations

---

Circuit Element	Differential Equation	Laplace Transform
Linear Constant Resistor Scale Factor	$v = R \cdot i$	$V(s) = R \cdot I(s)$
Linear Constant Inductor Differential Operator	$v = L \cdot \frac{di}{dt}$	$V(s) = s \cdot L \cdot I(s)$
Linear Constant Capacitor Integrator	$C \cdot \frac{dv}{dt} = i(t)$	$V(s) = \frac{1}{s \cdot C} \cdot I(s)$

- We ignore the Nonlinearity of the Switching by Treating the Switch States Separately

## Reminder: nth Order Linear Dif Eq Can Be Written As n-dimensional First Order Matrix Dif Eq

---

- **Standard Notation**

$$\frac{d}{dt} \mathbf{x} = \mathbf{A} \cdot \mathbf{x}(t) + \mathbf{B} \cdot \mathbf{u}(t)$$

$$\mathbf{y}(t) = \mathbf{C} \cdot \mathbf{x}(t) + \mathbf{D} \cdot \mathbf{u}(t)$$

- **Transfer Function**

$$\mathbf{X}(s) = (s\mathbf{I} - \mathbf{A})^{-1} \cdot [\mathbf{x}(0) + \mathbf{B} \cdot \mathbf{U}(s)]$$

$$\begin{aligned} \mathbf{Y}(s) &= \mathbf{C} \cdot \mathbf{X}(s) + \mathbf{D} \cdot \mathbf{U}(s) \\ &= \mathbf{C} \cdot (s\mathbf{I} - \mathbf{A})^{-1} \cdot \mathbf{x}(0) + \\ &\quad \left[ \mathbf{C} \cdot (s\mathbf{I} - \mathbf{A})^{-1} \cdot \mathbf{B} + \mathbf{D} \right] \cdot \mathbf{U}(s) \end{aligned}$$

$$\mathbf{G}(s) = \left[ \mathbf{C} \cdot (s\mathbf{I} - \mathbf{A})^{-1} \cdot \mathbf{B} + \mathbf{D} \right]$$

- **DC Solution**

$$\frac{d}{dt} \mathbf{x} = 0$$

$$\mathbf{X} = \mathbf{A}^{-1} \cdot \mathbf{B} \cdot U$$

$$\mathbf{Y} = \left[ \mathbf{C} \cdot \mathbf{A}^{-1} \cdot \mathbf{B} + \mathbf{D} \right] \cdot U$$

- **Buck Converter Definitions**


$$\mathbf{x}(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} = \begin{bmatrix} i_L(t) \\ v_C(t) \end{bmatrix}$$

$$\mathbf{u}(t) = v_i(t)$$

$$\begin{aligned} \mathbf{y}(t) &= v_o(t) = v_C(t) \\ &= \underbrace{\begin{bmatrix} 0 & 1 \end{bmatrix}}_{\mathbf{C}} \cdot \mathbf{x}(t) + \underbrace{\begin{bmatrix} 0 \end{bmatrix}}_{\mathbf{D}} \cdot \mathbf{u}(t) \end{aligned}$$


# Buck Converter Circuit: Converts from High to Low Voltage DC

---

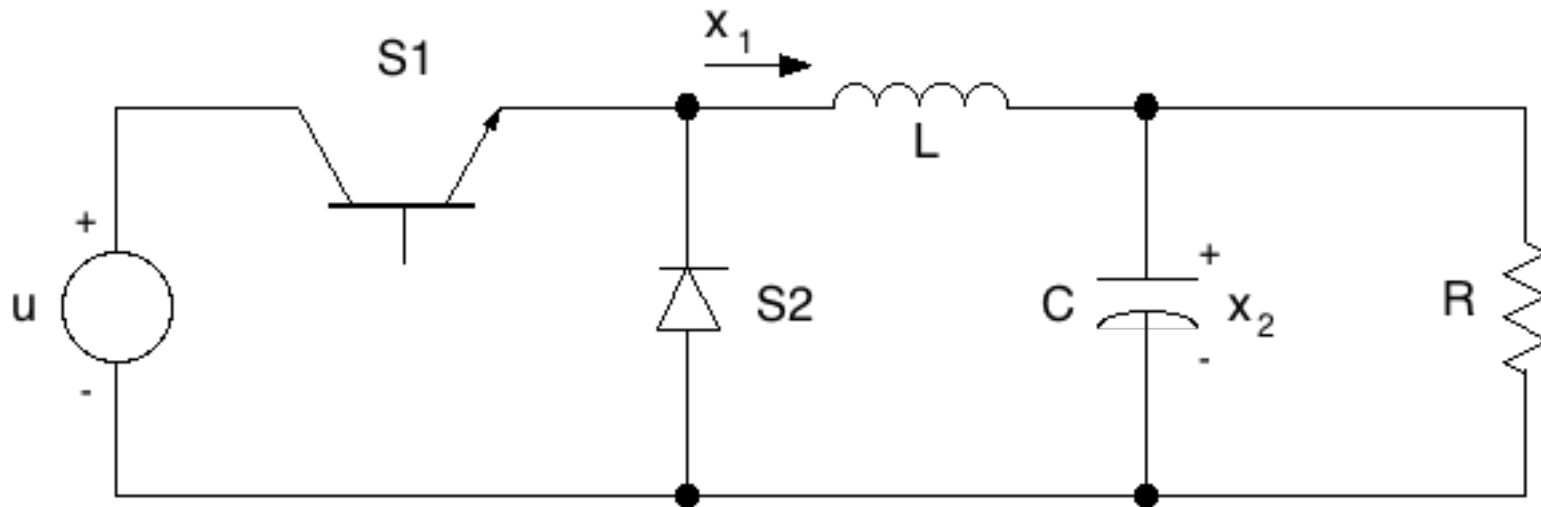



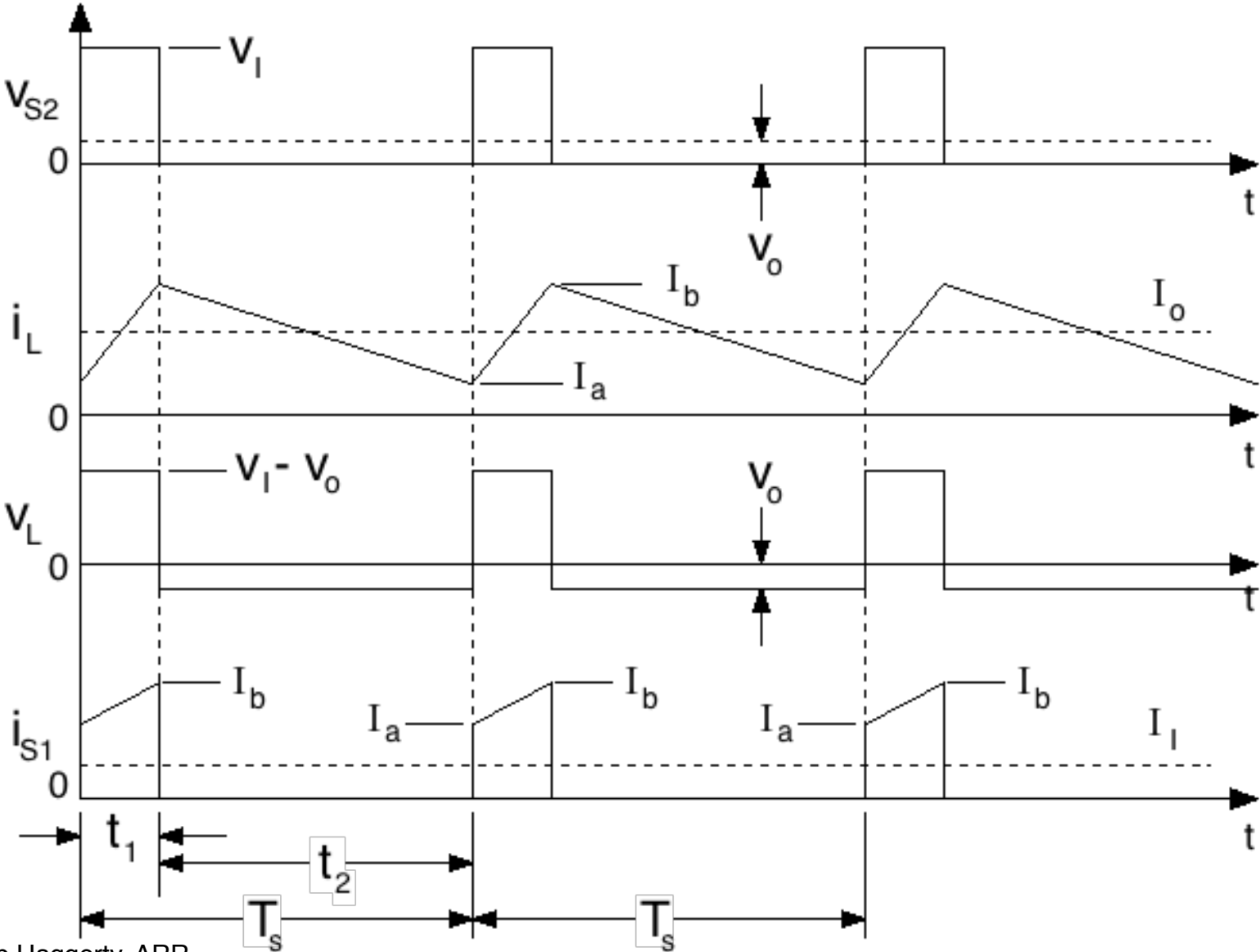
# Continuous Current Mode (CCM) Waveforms



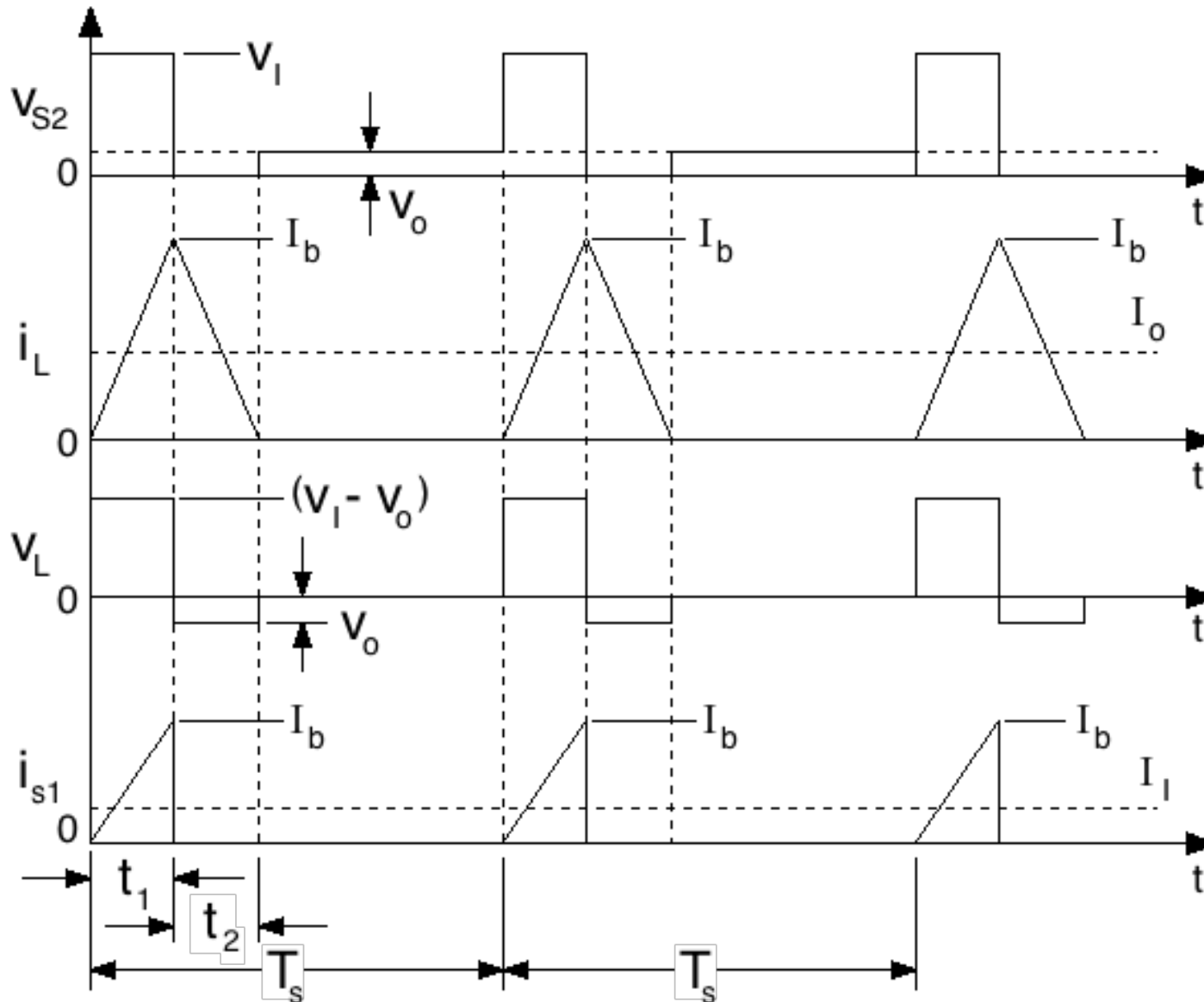
# Discontinuous Current Mode (DCM) Waveforms



# Case 1: Buck Converter Circuit

## S1 On and S2 Off

---

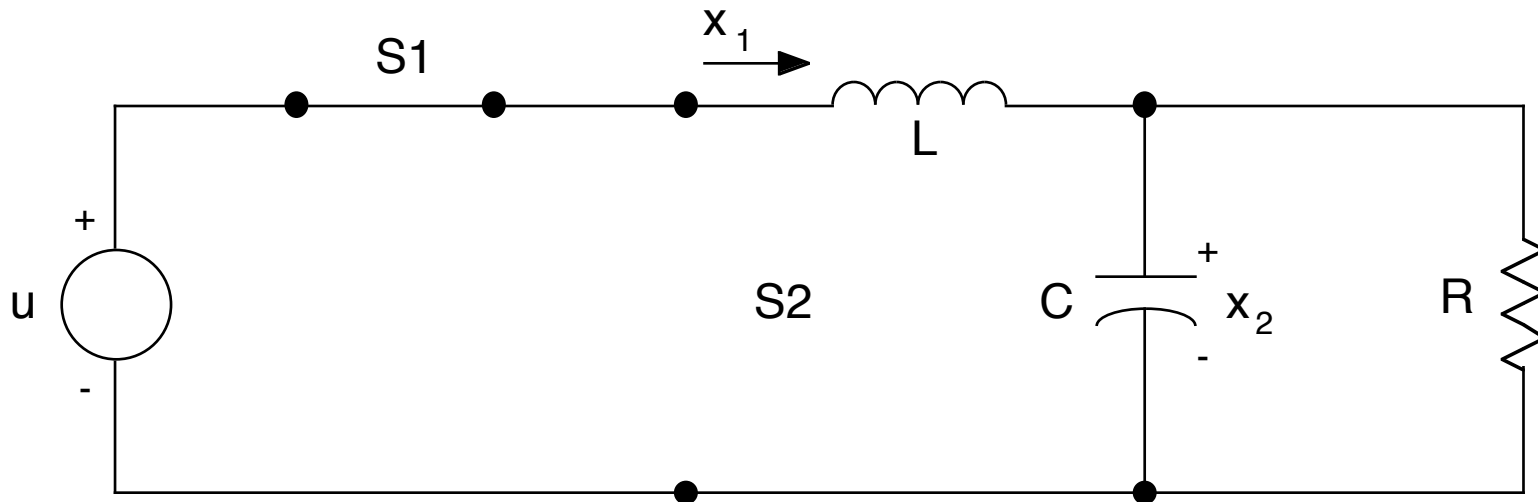

# Case 1: S1 On and S2 Off for CCM and DCM

- **Circuit Equations**

$$v_i(t) = L \cdot \frac{d}{dt} i_L(t) + v_C(t)$$

$$C \cdot \frac{d}{dt} v_C = i_L(t) - \frac{v_C(t)}{R}$$

- **In State Variables**

$$u(t) = L \cdot \frac{d}{dt} x_1 + x_2(t)$$

$$C \cdot \frac{d}{dt} x_2 = x_1(t) - \frac{1}{R} \cdot x_2(t)$$

- **Rearranging**

$$\frac{d}{dt} x_1 = -\frac{1}{L} \cdot x_2(t) + \frac{1}{L} \cdot u(t)$$


$$\frac{d}{dt} x_2 = \frac{1}{C} \cdot x_1(t) - \frac{1}{R \cdot C} \cdot x_2(t)$$

- **State Model**

$$\frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{R \cdot C} \end{bmatrix}}_{\mathbf{A}_1} \cdot \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \underbrace{\begin{bmatrix} 1/L \\ 0 \end{bmatrix}}_{\mathbf{B}_1} \cdot [u(t)]$$

## Case 2: Buck Converter Circuit S1 Off and S2 On

---

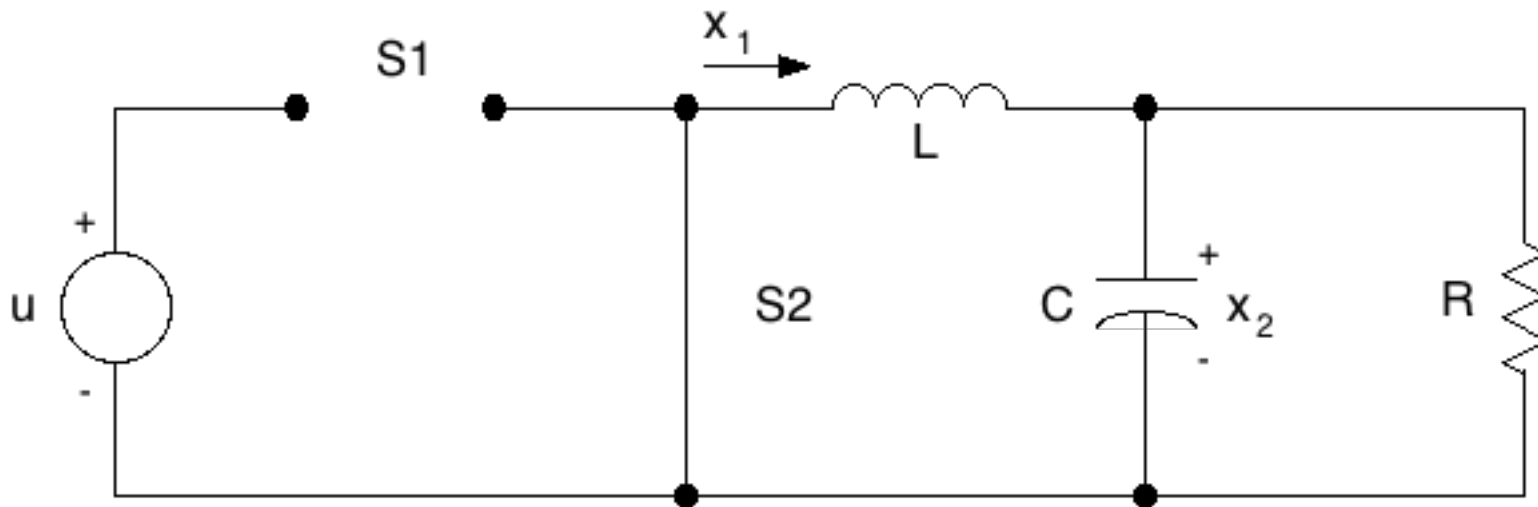

## Case 2: S1 Off and S2 On for CCM and DCM

- Circuit Equations**

$$0 = L \cdot \frac{d}{dt} i_L(t) + v_C(t)$$

$$C \cdot \frac{d}{dt} v_C = i_L(t) - \frac{v_C(t)}{R}$$

- In State Variables**

$$0 = L \cdot \frac{d}{dt} x_1 + x_2(t)$$

$$C \cdot \frac{d}{dt} x_2 = x_1(t) - \frac{1}{R} \cdot x_2(t)$$

- Rearranging**

$$\frac{d}{dt} x_1 = -\frac{1}{L} \cdot x_2(t)$$


$$\frac{d}{dt} x_2 = \frac{1}{C} \cdot x_1(t) - \frac{1}{R \cdot C} \cdot x_2(t)$$

- State Model**

$$\frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{R \cdot C} \end{bmatrix}}_{\mathbf{A}_2} \cdot \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{B}_2} \cdot [u(t)]$$

## Case 3: Buck Converter Circuit S1 Off and S2 Off

---

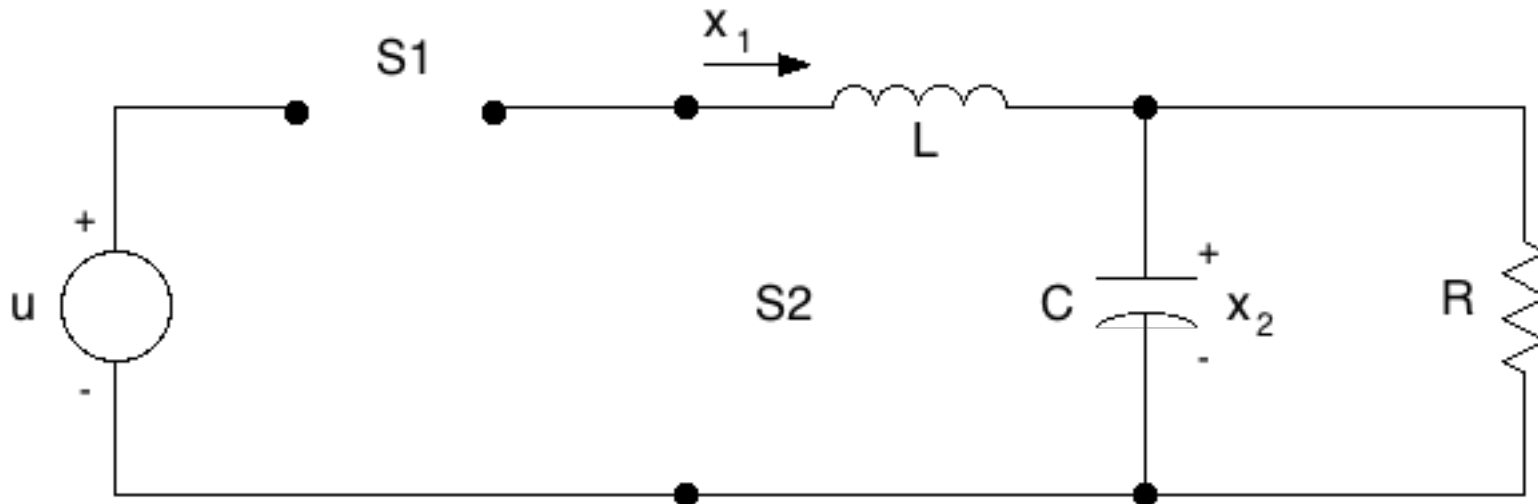

## Case 3: S1 Off and S2 Off for DCM Only

---

- Circuit Equations**

$$i_L(t) = 0 \Rightarrow \frac{d}{dt} i_L(t) = 0$$

$$C \cdot \frac{d}{dt} v_C = 0 - \frac{v_C(t)}{R}$$

- In State Variables**

$$\frac{d}{dt} x_1 = 0$$

$$C \cdot \frac{d}{dt} x_2 = 0 - \frac{1}{R} \cdot x_2(t)$$

- Rearranging**

$$\frac{d}{dt} x_1 = 0$$

$$\frac{d}{dt} x_2 = 0 \cdot x_1(t) - \frac{1}{R \cdot C} \cdot x_2(t)$$

- State Model**

$$\frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 0 \\ 0 & -\frac{1}{R \cdot C} \end{bmatrix}}_{\mathbf{A}_3} \cdot \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{B}_3} \cdot [u(t)]$$



# State Space Averaged System of Equations for CCM and DCM

- CCM

$$\frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{R \cdot C} \end{bmatrix} \cdot \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} d/L \\ 0 \end{bmatrix} \cdot [u(t)]$$

$$\mathbf{B}(d) = d \mathbf{B}_1 + (1 - d) \mathbf{B}_2$$

$$\mathbf{A}(d) = d \mathbf{A}_1 + (1 - d) \mathbf{A}_2$$

- DCM

$$\frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} 0 & -\frac{d_1 + d_2}{L} \\ \frac{d_1 + d_2}{C} & -\frac{1}{R \cdot C} \end{bmatrix} \cdot \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} d_1/L \\ 0 \end{bmatrix} \cdot [u(t)]$$

$$\mathbf{B}(d_1, d_2) = d_1 \mathbf{B}_1 + d_2 \mathbf{B}_2 + (1 - d_1 - d_2) \mathbf{B}_3$$

$$\mathbf{A}(d_1, d_2) = d_1 \mathbf{A}_1 + d_2 \mathbf{A}_2 + (1 - d_1 - d_2) \mathbf{A}_3$$

# Averaged CCM State Space Model: Linearization by Small Signal Analysis

---

- **Small Signal Equations**

$$\mathbf{x} = \overset{\text{DC}}{X} + \overset{\text{AC}}{\chi}$$

$$\mathbf{u} = U + \mu$$

$$d = D + \delta$$

- **After Some Algebra**

$$\frac{d}{dt} \mathbf{x} = \mathbf{A}(D) \cdot \mathbf{x} + \mathbf{B}(D) \cdot \mathbf{u} + \mathbf{E}_{12} \cdot \delta$$

$$\text{where: } \mathbf{E}_{12} = (\mathbf{A}_1 - \mathbf{A}_2) \cdot X + (\mathbf{B}_1 - \mathbf{B}_2) \cdot U$$

- **Substitute and Expand**

$$\frac{d}{dt} \mathbf{x} = \frac{d}{dt} X + \frac{d}{dt} \chi = \frac{d}{dt} \chi \quad \text{dc Solution}$$

$$= \mathbf{A}(D) \cdot X + \mathbf{B}(D) \cdot U$$

$$+ \mathbf{A}(D) \cdot \chi + \mathbf{B}(D) \cdot \mu$$

$$= \mathbf{A}(\delta) \cdot X + \mathbf{B}(\delta) \cdot U$$

~~$$+ \mathbf{A}(\delta) \cdot \chi + \mathbf{B}(\delta) \cdot \mu$$~~

Neglect ac Cross Terms

# Averaged DCM State Space Model: Linearization by Small Signal Analysis

---

- **Small Signal Equations**

$$\mathbf{x} = \overset{\text{DC}}{X} + \overset{\text{AC}}{\chi}$$

$$\mathbf{u} = U + \mu$$

$$d_1 = D_1 + \delta_1$$

$$d_2 = D_2 + \delta_2$$

- **Substitute and Expand**

$$\frac{d}{dt} \mathbf{x} = \frac{d}{dt} X + \frac{d}{dt} \chi = \frac{d}{dt} \chi$$

$$= \mathbf{A}(D_1, D_2) \cdot X + \mathbf{B}(D_1, D_2) \cdot U \quad \leftarrow \text{dc Solution}$$

$$+ \mathbf{A}(D_1, D_2) \cdot \chi + \mathbf{B}(D_1, D_2) \cdot \mu \quad \leftarrow \text{ac Approx}$$

$$+ \mathbf{A}(\delta_1, \delta_2) \cdot X + \mathbf{B}(\delta_1, \delta_2) \cdot U$$

$$+ \mathbf{A}(\delta_1, \delta_2) \cdot \chi + \mathbf{B}(\delta_1, \delta_2) \cdot \mu \quad \leftarrow \text{Neglect ac Cross Terms}$$

- **After Some Algebra**

$$\frac{d}{dt} \mathbf{x} = \mathbf{A}(D_1, D_2) \cdot \mathbf{x} + \mathbf{B}(D_1, D_2) \cdot \mathbf{u} \\ + \mathbf{E}_{13} \cdot \delta_1 + \mathbf{E}_{23} \cdot \delta_2$$

where :

$$\mathbf{E}_{13} = (\mathbf{A}_1 - \mathbf{A}_3) \cdot X + (\mathbf{B}_1 - \mathbf{B}_3) \cdot U$$

$$\mathbf{E}_{23} = (\mathbf{A}_2 - \mathbf{A}_3) \cdot X + (\mathbf{B}_2 - \mathbf{B}_3) \cdot U$$

## Now Let's Get Specific

- **Component Values**

$$U = V_I = 10 \text{ Volts}$$

$$V_O = 5 \text{ Volts}$$

$$L = 100 \mu\text{H}$$

$$C = 1,000 \mu\text{F}$$

$$T_S = 10 \mu\text{s}$$

$$R = \left\langle \begin{array}{ll} 1 \Omega & CCM \\ 100 \Omega & DCM \end{array} \right\rangle$$

- **Thus**

$$M = \frac{V_O}{V_I} = 0.5$$

$$\tau_{LC} = \frac{1 - M}{2} = 0.25$$

$$\tau_L = \frac{L}{R \cdot T_S} = \left\langle \begin{array}{ll} 10 > \tau_{LC} & CCM \\ 0.1 < \tau_{LC} & DCM \end{array} \right\rangle$$

## The DC Solution is:

- **CCM**

$$D = M = 0.5$$

$$U = V_I = 10$$

$$X = \begin{bmatrix} I_L \\ V_C \end{bmatrix} = \begin{bmatrix} D/R \\ D \end{bmatrix} \cdot V_I = \begin{bmatrix} 5 \\ 5 \end{bmatrix}$$

- **DCM**

$$D_1 = M \sqrt{\frac{2 \cdot \tau_L}{1 - M}} = 0.316$$

$$D_2 = \sqrt{2 \cdot \tau_L \cdot (1 - M)} = 0.316$$

$$U = V_I = 10$$

$$X = \begin{bmatrix} I_L \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{D_1}{(D_1 + D_2)^2 \cdot R} \\ \frac{D_1}{D_1 + D_2} \end{bmatrix} \cdot V_I = \begin{bmatrix} 7.91 \\ 5 \end{bmatrix}$$

# The Open Loop Transfer Function Is:

- **The CCM Transfer Functions Are:**

$$G_b(s) = 0.5 \frac{1 - 2 \cdot 10^{-3} \cdot s}{1 - 1.6 \cdot 10^{-3} \cdot s}$$

$$G_e(s) = \frac{1 - 2 \cdot 10^{-3} \cdot s}{1 - 1.6 \cdot 10^{-3} \cdot s}$$

- **Feedback is Unity**

$$H(s) = 1$$

- **Throw in Pure Time Delay**

$$G_d(s) = e^{-s \cdot T_d}$$

- **Use First Order Controller Simple Integrator**

$$G_c(s) = k \frac{1}{s}$$

- **Open Loop Transfer Function Is:**

$$\begin{aligned} GH(s) &= G_c(s) \cdot G_e(s) \cdot G_d(s) \cdot H(s) \\ &= k \frac{1}{s} \cdot \frac{1 - 2 \cdot 10^{-3} \cdot s}{1 - 1.6 \cdot 10^{-3} \cdot s} \cdot e^{-s \cdot T_d} \end{aligned}$$

- **Now We Can Do Some Bode Plots**

# Linearized Averaged State Space Model Enables Use of Modern Algorithms

---

- **One Such Algorithm is the Kalman Filter**
  - **Powerful Estimation Method**
  - **Linear unbiased minimum variance estimate**
  - **Maximum likelihood estimate (Linear and Gaussian)**
  - **Works on steadily expanding set of data**
  - **Recursive**
- **Where Would One Be Used**
  - **Estimate States for Feedback Control**
  - **For Buck Converter**
    - » **Inductor Current (Running Average)**
- **The Next Few Charts Provide a Brief Intro to the Equations for the Discrete Time Kalman Filter**

# Discrete Time Model of Plant

---

$$\mathbf{x}_{n+1} = \Phi(n+1, n)\mathbf{x}_n + \mathbf{B}_n u_n + \mathbf{G} \mathbf{N}_n^s$$

$$z_n = \mathbf{H}_n \mathbf{x}_n + \mathbf{R}^{1/2} \mathbf{N}_n^z$$

$$\mathbb{E}[\mathbf{N}_n^s] = \mathbf{0}$$

$$\mathbb{E}[\mathbf{N}_n^s \mathbf{N}_m^{sT}] = \mathbf{I} \delta_{nm}$$

$$\mathbb{E}[\mathbf{N}_n^z] = \mathbf{0}$$

$$\mathbb{E}[\mathbf{N}_n^z \mathbf{N}_m^{zT}] = \mathbf{I} \delta_{nm}$$



# Kalman Filter Equations (Recursive)

---

Gain:  $K_n = P_{p_n} H'_n [H_n P_{p_n} H'_n + R_n]^{-1}$

Filter:  $x_{f_n} = x_{p_n} + K_n (z_n - H_n x_{p_n})$

Prediction:  $x_{p_{n+1}} = \Phi(n+1, n) x_{f_n} + B_n u_n$

Filter Cov.:  $P_{f_n} = [I - K_n H_n] P_{p_n}$

Prediction:  $P_{p_n} = \Phi(n+1, n) P_{f_n} \Phi(n+1, n)^T + Q$

where:  $x_{f_n} = \hat{x}_{n|n} = E[x_n | z_n, \dots, z_1]$

$$x_{p_n} = \hat{x}_{n|n-1} = E[x_n | z_{n-1}, \dots, z_1]$$

$$P_{f_n} = \text{Cov}(x_n - \hat{x}_{n|n}) = E[(x_n - \hat{x}_{n|n})(x_n - \hat{x}_{n|n})^T]$$

$$P_{p_n} = \text{Cov}(x_n - \hat{x}_{n|n-1}) = E[(x_n - \hat{x}_{n|n-1})(x_n - \hat{x}_{n|n-1})^T]$$

# Initialization Case 1: Know Initial Mean and Cov

---

$$\bar{x} = E[x_0]$$

$$P_0 = \text{Cov}(x_0 - \bar{x}_0) = E[(x_0 - \bar{x}_0)(x_0 - \bar{x}_0)^T]$$

$$\text{Set } x_p = \bar{x}_0$$

$$P_p = P_0$$

Then run filter

## Initialization Case 2: No A Priori Information

---

Set :  $x_f = f1(z_0, \dots)$

$$P_f = f2(R)$$

Then compute :

$$x_p = \Phi x_f + B u_0$$

$$P_p = \Phi P_f \Phi^T + Q$$

Then run filter

$f1(z_0, \dots)$  maps measurement(s) to state

$f2(R)$  maps measurement cov to filter cov

Note: May want to guess some values rather than collecting several estimates to “measure” full set of states.